

Heaven's Light is Our Guide
Rajshahi University of Engineering and Technology



Course Code
ECE 2208

Course Title
Electrical Machines - I Sessional

Experiment Date: December 6, 2023,
Submission Date: December 20, 2023

Lab Report 5: Blocked rotor test & no-load test of 3-phase induction motor and determination of circuit parameters.

Submitted to
Md. Omaer Faruq Goni
Lecturer
Dept of ECE, RUET

Submitted by
Md. Tajim An Noor
Roll: 2010025

Constructing of three phase transformer using three single phase transformers & observing line & phase voltage relation in primary and secondary windings.

1 Introduction

Three phase motor

Circuit Diagrams

Figure 1: Circuit diagrams for Y- Δ three transformer connection.

2 Tools Used

- Three Phase Motor, (220/440V, 9.1/4.55A)
- Ammeter (0A - 5A)
- Voltmeter (0V - 120V)
- Wattmeter
- Three Phase AC supply (220V)
- Three phase Variac (0-250V)
- Connecting wires

3 Data & Calculation

3.1 Data Table:

Table 1: Y Connection

V_{an}	V_{bn}	V_{cn}	V_{AB}	V_{BC}	V_{CA}
100.8	100.7	101.5	175.8	176.8	177.4

Table 2: Δ Connection

V_{an}	V_{AB}
150.6	131.7

3.2 Calculation:

For Y-connection,

$$V_L = \sqrt{3}V_P$$

Line Voltage,

$$V_{an} = 100.8V$$

\therefore Phase voltage,

$$V_{AB} = \sqrt{3} \times 100.8 = 174.59$$

Average Measured phase voltage,

$$V_{AB} = \frac{175.8 + 176.8 + 177.4}{3} = 176.67V$$

For Δ -connection,

$$V_L = V_P$$

Line voltage,

$$V_{an} = 100.7V$$

Measured phase voltage,

$$V_{AB} = 100.7V$$

4 Discussion

Just like three phase supply, in transformers, the relation persists. In wye connection, the line & phase voltages aren't the same but in delta connection, they are the same.

5 Conclusion

Since this experiment was done with AC supply, utmost caution was exercised to avoid any accident. Additionally, the line and phase current relation wasn't tested as it'd require precise and cautious connection. To avoid any dangers, only the voltage relation was done in this experiment.